

Designing the processor

Datapath and Control Signals

➤ [Click here](#)

Instruction Set

There are 31 instructions that can be used by the assembly programmer. Some instructions have a 16-bit operand, and most instructions are zero operand instructions. 8 bits are used for opcode. Following table explains the operations of each instruction.

Instruction	Opcode	Operand (16 bit)	Operation
loadac	0000 0100	-	ac <= DM[ac]
movacr	0000 1000	-	r <= ac
movacr1	0000 1001	-	r1 <= ac
movacr2	0000 1010	-	r2 <= ac
movacr3	0000 1011	-	r3 <= ac
movacr4	0000 1100	-	r4 <= ac
movacr5	0000 1101	-	r5 <= ac
movacdar	0000 1110	-	dar <= ac
movrac	0000 1111	-	ac <= r
movr1ac	0001 0000	-	ac <= r1
movr2ac	0001 0001	-	ac <= r2
movr3ac	0001 0010	-	ac <= r3
movr4ac	0001 0011	-	ac <= r4
movr5ac	0001 0100	-	ac <= r5
movdarac	0001 0101	-	ac <= dar
stac	0001 0110	-	DM[ac] <= ac
add	0001 1001	-	ac <= ac + r
sub	0001 1011	-	ac <= ac - r
lshift	0001 1101	-	ac <= r << ac
rshift	0001 1111	-	ac <= r >> ac
incac	0010 0001	-	ac <= ac + 1
incdar	0010 0010	-	dar <= dar + 1
incr1	0010 0011	-	r1 <= r1 + 1
incr2	0010 0100	-	r2 <= r2 + 1
incr3	0010 0101	-	r3 <= r3 + 1
loadim	0010 0110	imm	ac <= imm
jumpz	0010 1001	imm	if z == 1, go to instruction IM[imm]
jumpnz	0011 0000	imm	if z == 0, go to instruction IM[imm]
jump	0011 0001	imm	go to instruction IM[imm]
nop	0011 0010	-	no operation
endop	0011 0011	-	end process

Microinstructions

These microinstructions are used for finite state machine in the control unit. one microinstruction can be operated in one clock cycle. Following table explains operations of each microinstruction.

Instruction (8bits)	Opcode (decimal)	Microinstruction (6bits)	Operation
idle (internal)	-	idle	goto fetch1 if status == 1 else idle
fetch (internal)	-	fetch1	read IMEM
			write ir
			goto fetch2
		fetch2	read IMEM
			write ir
		fetch3	goto fetch3
			read IMEM
loadac	4	loadac1	goto ir[5:0]
			read ac
			write dar
		loadac2	goto loadac2
			read ac
			wirte dar
		loadac3	goto loadac3
			read DMEM
			write ac
		loadac4	goto loadac4
			read DMEM
			write ac
movacr	8	movacr	increment pc
			goto fetch1
			read ac
			write r
movacr1	9	moveacr1	increment pc
			goto fetch1
			read ac
			write r1
movacr2	10	moveacr2	increment pc
			goto fetch1
			read ac
			write r2
movacr3	11	moveacr3	increment pc
			goto fetch1
			read ac
			write r3
movacr4	12	moveacr4	increment pc
			goto fetch1

			write r4
			increment pc
			goto fetch1
movacr5	13	moveacr5	read ac
			write r5
			increment pc
			goto fetch1
movacdar	14	moveacdar	read ac
			write dar
			increment pc
			goto fetch1
movrac	15	moverac	read r
			write ac
			increment pc
			goto fetch1
movr1ac	16	mover1ac	read r1
			write ac
			increment pc
			goto fetch1
movr2ac	17	mover2ac	read r2
			write ac
			increment pc
			goto fetch1
movr3ac	18	mover3ac	read r3
			write ac
			increment pc
			goto fetch1
movr4ac	19	mover4ac	read r4
			write ac
			increment pc
			goto fetch1
movr5ac	20	mover5ac	read r5
			write ac
			increment pc
			goto fetch1
movdarac	21	movedarac	read dar
			write ac
			increment pc
			goto fetch1
stac	22	stac1	read ac
			goto stac2
		stac2	read ac
			write dm
			goto stac3
		stac3	read ac
			increment pc
			goto fetch1

add	25	add1	add alu
			goto add2
		add2	add alu
			write alu_to_ac
			increment pc
sub	27	sub1	goto fetch1
			sub alu
		sub2	goto sub2
			sub alu
			write alu_to_ac
lshift	29	lshift1	increment pc
			goto fetch1
		lshift2	lshift alu
			write alu_to_ac
			increment pc
rshift	31	rshift1	goto fetch1
			rshift alu
		rshift2	goto rshift2
			rshift alu
			write alu_to_ac
incac	33	incac	increment pc
			increment ac
			goto fetch1
incdar	34	incdar	incrementtnt pc
			increment dar
			goto fetch1
incr1	35	incr1	increment r1
			incrementtnt pc
			goto fetch1
incr2	36	incr2	increment r2
			incrementtnt pc
			goto fetch1
incr3	37	incr3	increment r3
			incrementtnt pc
			goto fetch1
loadim	38	loadim1	increment pc
			goto loadim2
		loadim2	read IMEM
			goto loadim3
		loadim3	read IMEM
			write ac
			increment pc
			goto fetch1

jump	49	jump	increment pc goto jumpz2
jumpz	41	jumpz1	increment pc goto jumpz2 if z == 1 else jumpz6
		jumpz2	read IMEM write pc goto jumpz3
		jumpz3	read IMEM write pc goto jumpz4
		jumpz4	read IMEM write ir goto jumpz5
		jumpz5	read IMEM write ir goto fetch3
		jumpz6	goto jumpz7
		jumpz7	increment pc goto jumpz4
jumpnz	48	jumpnz1	increment pc goto jumpz3 if z == 0 else goto jumpz7
endop	51	endop	read DMEM goto endop
nop	50	nop	increment pc goto fetch1

Finite State Machines for Microinstructions

➤ [Click here](#)


Modules and Components

Machine

There are three phases in this machine.

 1. Load the image – Phase 1
2. Processing – Phase 2
3. Get the processed image – Phase 3

In phase 1, we have to give the image data to data_in and memory address to data_addr_in. Then processing will be done. After phase 2 is done, end_process will be asserted. In phase 3, we can get the output image data from the data_out.



Inputs

clk – clock

status – control signal for change phases (input image data, process data, output data)

data_in – input image data

data_addr_in – input data memory address


Outputs

end_process – signal that indicate process has ended


data_out – output image data

status	10	01	11
phase	1 – load image	2 – process	3 – output image

Inside of the machine

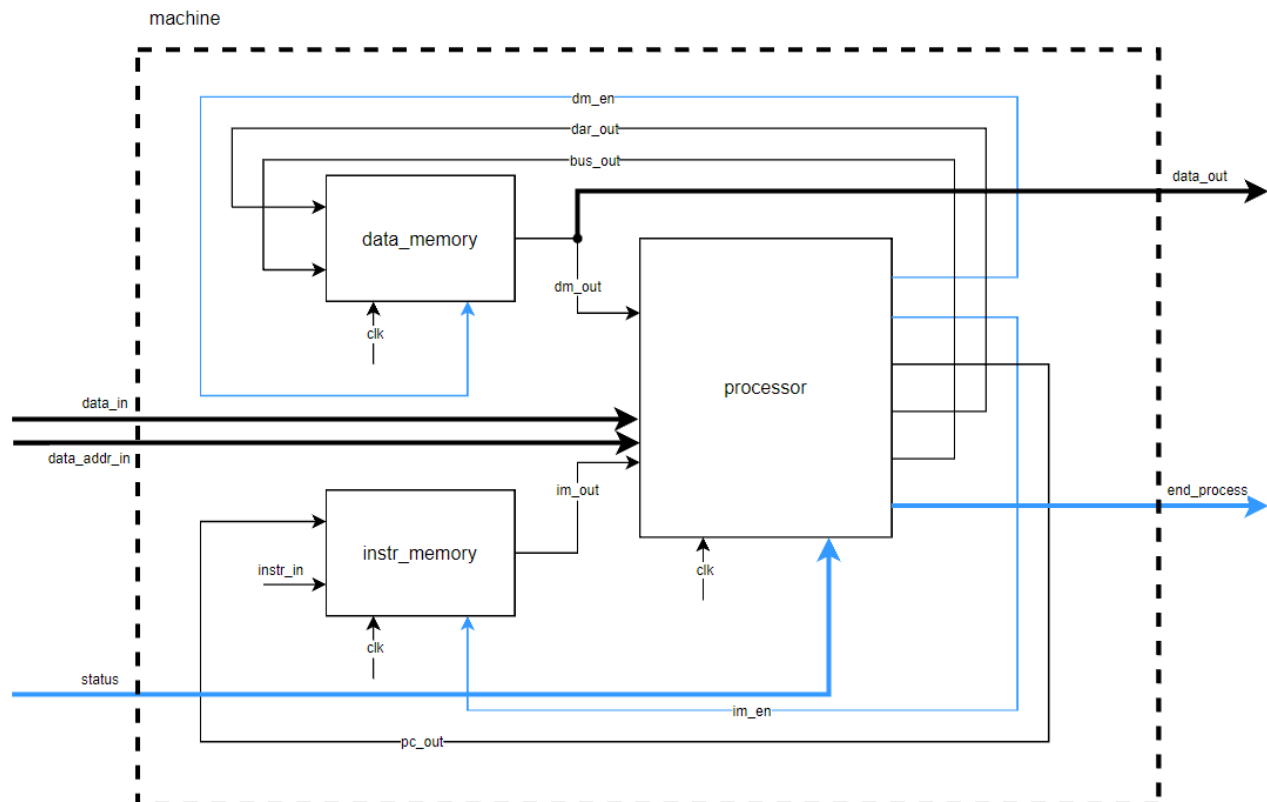

Processor

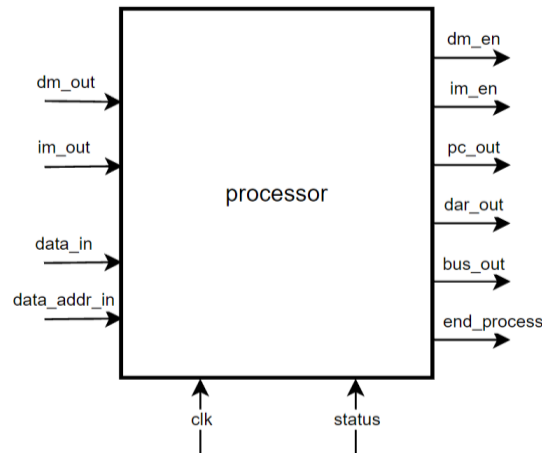

Inputs

clk – clock

status – control signal for change phases (input image data, process data, output data)

dm_out – output of data memory

im_out – output of instruction memory

data_in – input image data

data_addr_in – input data memory address

Outputs

end_process – signal that indicate process has ended

dm_en – data memory write enable signal

im_en – instruction memory write enable signal

pc_out – instruction memory address

dar_out – data memory address

bus_out – data output for data memory

- Inside of the Processor – [Click here](#)

Modules Inside the Processor

Arithmetic & Logic Unit (ALU) – Do arithmetic and logic operations in the processor

Control Unit – Do all the controlling in the processor. Implemented as a finite state machine.

Special purpose registers


- Accumulator (ac) – input for the ALU, store ALU output
- Program counter (pc) – directed to the next instruction to be fetched
- Instruction register (ir) – store the instruction fetched from the instruction memory
- Data address register (dar) – keep the address of the store location of the data memory. Loading from data memory and storing to data memory are being done using this address
- r register – one of the inputs for the ALU

General purpose registers

- r1, r2, r3 – general purpose registers which can be incremented
- r4, r5 – general purpose registers which cannot be incremented

ALU

 
ALU is responsible for all the arithmetic and logic operations. Inputs are taken from ac and r registers and output is stored in ac register. We are using 3-bit alu_op even though there are only four operations since it is better to have some improvement capabilities. z will be 1 if the alu_out is zero. z will be 0 if the alu_out is nonzero.



alu_op	Operation	Description
001	Addition	$\text{Alu_out} \leq \text{in1} + \text{in2}$
010	Subtraction	$\text{Alu_out} \leq \text{in2} - \text{in1}$
011	Left shift	$\text{Alu_out} \leq \text{in1} \ll \text{in2}$
100	Right shift	$\text{Alu_out} \leq \text{in1} \gg \text{in2}$

Control Unit

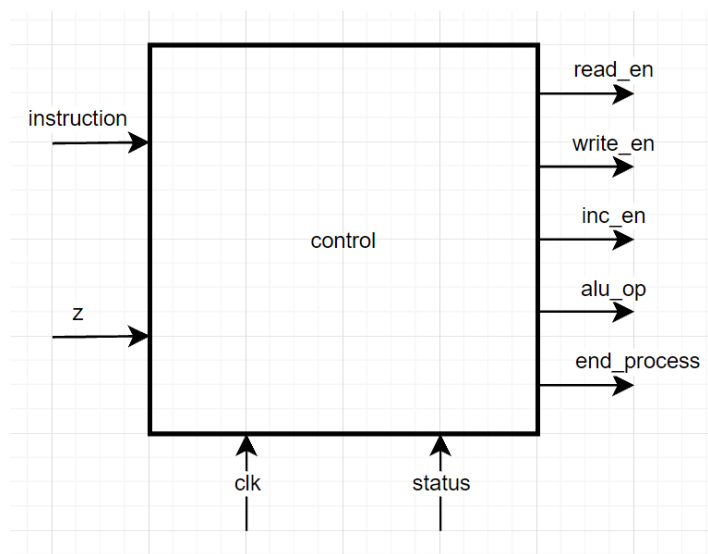Control Unit is responsible for all the control signals in the processor. Here we are implemented this using a finite state machine.



Inputs	Outputs
clk – clock	end_process – signal that indicate process has ended
status – control signal for change phases (input image data, process data, output data)	read_en – 4 bit read enable signal
instruction – instruction from the instruction register	write_en – 16 bit write enable signal
z – z output from the alu	inc_en – 8 bit increment enable signal
	alu_op – ALU opcode

Read Enable – read_en

read_en is the control signal that is responsible for all the readings in the processor. Read values are written to the data bus. We cannot read from multiple registers and write them to the same bus. Hence, we are using 4 bit signal such that only one register can be read at one time.

Decimal Value	Register
0	-
1	dar
2	ac
3	r
4	r1
5	r2
6	r3
7	r4
8	r5
9	DM
10	IM

Write Enable – write_en

write_en is the control signal that is responsible for all the writings in the processor. Unlike the reading, we can write data to multiple locations at the same time. Therefore, we are using 16-bit signal and each bit has assigned to separate location. We can write those location by setting those bits to 1.

Bit 15	Bit 14	Bit 13	Bit 12	Bit 11	Bit 10	Bit 9	Bit 8	Bit 7	Bit 6	Bit 5	Bit 4	Bit 3	Bit 2	Bit 1	Bit 0
N/A	N/A	alu to ac	IM	DM	r1	r2	r3	r4	r5	r	ac	ir	dar	pc	N/A


Increment Enable – *inc_en*

inc_en is the control signal that is responsible for all the increments in the processor. Same as the writing, we can increment multiple registers at the same time.

Bit	Bit	Bit	Bit	Bit	Bit	Bit	Bit
7	6	5	4	3	2	1	0
N/A	r3	r2	r1	dar	ac	pc	N/A


Accumulator

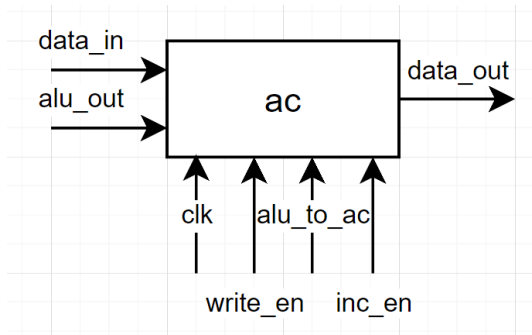Accumulator is a special purpose register which has two data inputs. One is from the data bus and the other one is from the ALU output. There are two write enable signals to indicate from which input the writing should be done. This is one of the inputs to the ALU.




Register Which Can Be Incremented

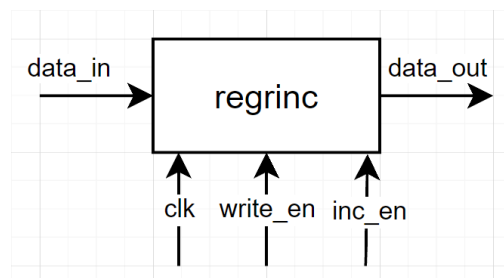pc, dar, r1, r2, r3 are registers of this type. The values in those registers can be incremented without using the ALU.




Register Which Cannot Be Incremented

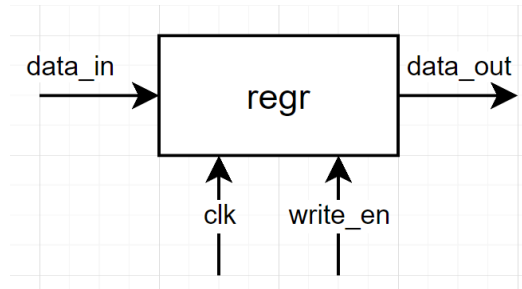ir, r, r4, r5 are registers of this type. The values in those registers cannot be incremented without using the ALU.




Data Bus

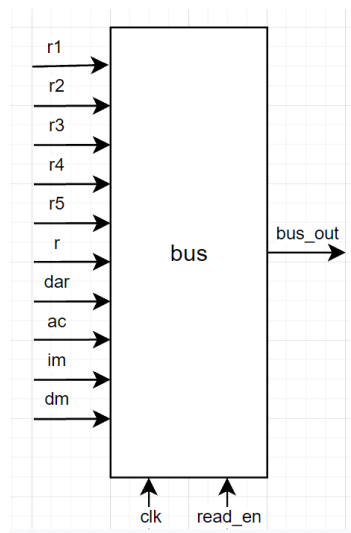This is a 16-bit path which connects all the necessary components that needed to the data flow.



Data Memory

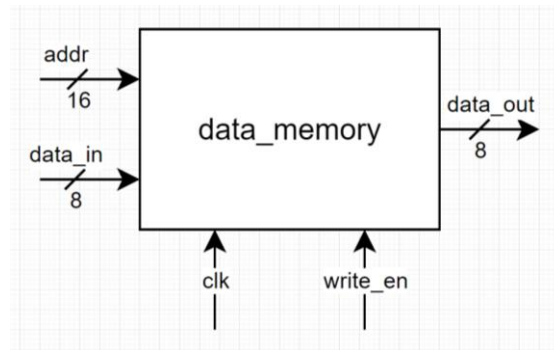This is the main memory which data is stored. The image should be stored here before the processing begins. This memory contains 65536 locations of 8 bits long. Since we are using 256*256 image, 65536 pixel values are needed to be stored and that is why 65536 locations. Since the pixel value range is 0-255, we need 8-bit long memory to store that.



Instruction Memory

This is for storing the instructions. This is a read only memory. The processor cannot write into instruction memory during the processing. This can be written only when we need to load a new programme.

